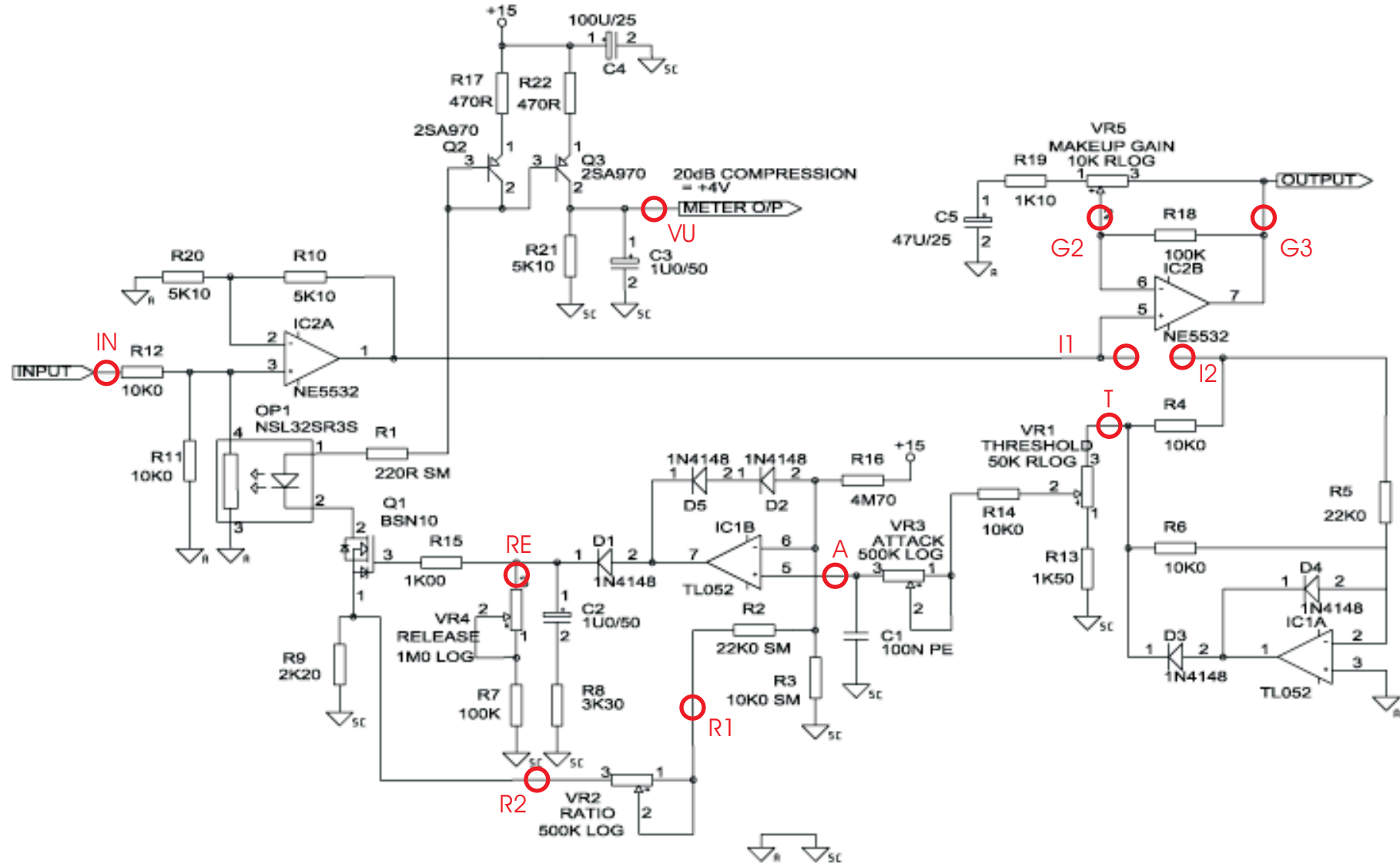


<http://www1.silonex.com/audiohm/compressor.html>




Opto-compressor

Schematic by Silonex


<http://www1.silonex.com/audiohm/compressor.html>

PCB = 48x55mm

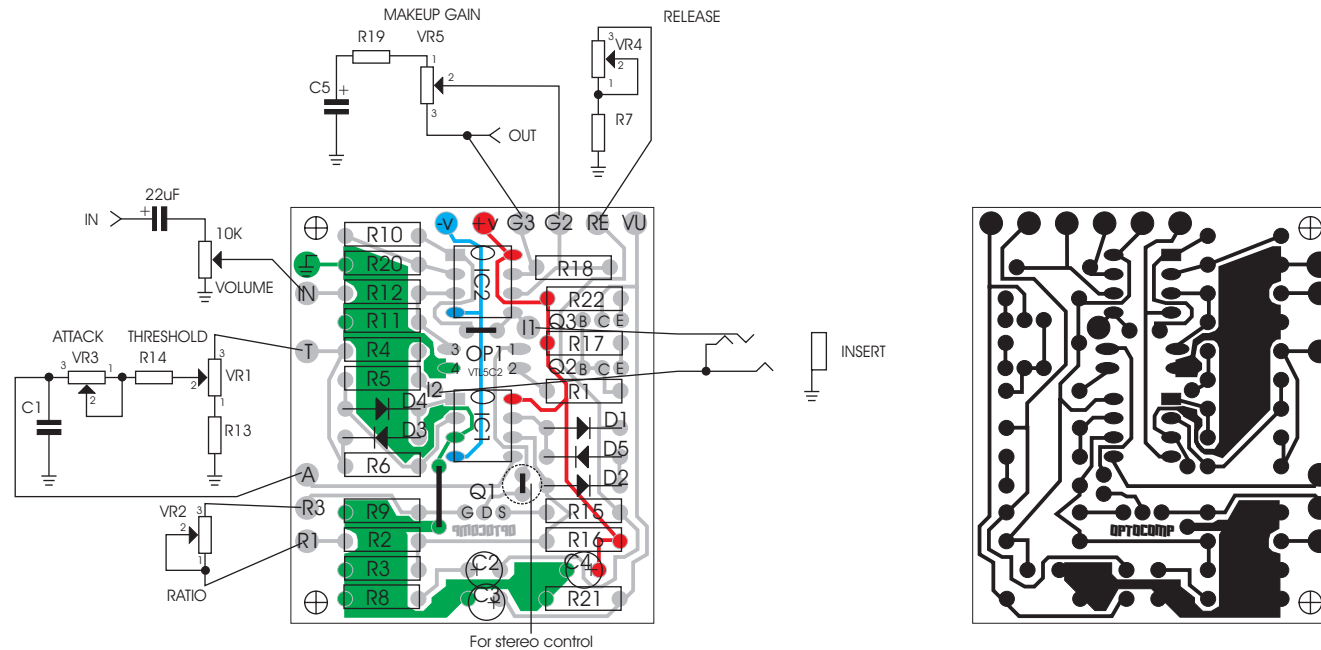

Original components, IC1 = TL052, IC2 = NE5532, OP1 = NSL32SR3S, Q1 = BSN10, Q2 & Q3 = 2SA970.

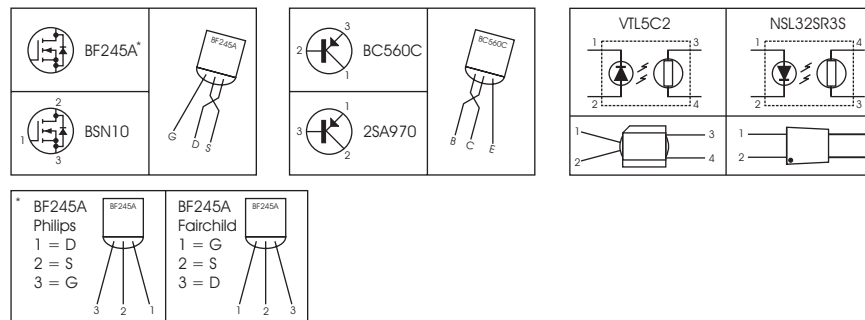My replacement, IC1 = TL072, OP1 = VTL5C2, Q1 = BF245A, Q2 & Q3 = BC560C.



OP1 pin 3 and 4 are reversed on the PCB, compared to the schematic.