

Radio— Electronics

**ELECTRONIC DEVICES
FOR SELF-IMPROVEMENT**

\$1.25 MAY 1980

**Put your cap meter to better use
What happened at WARC-79
Build a \$125 triggered scope**

**Dial-up network for home computers
Inside the Beta video recorder
Build a wide-range audio generator**



**BUILD THIS
PROFESSIONAL
DRUM SYNTHESIZER**



BUILD THIS

the DRUM...



A PERCUSSION SYNTHESIZER

*For the musician and musician to be.
This unique 4-channel synthesizer adds more than
just a beat to your music.*

STEVE WOOD

PERCUSSION SYNTHESIS SEEMS TO BE growing more popular daily. The trouble is, it's expensive! Or it was. Building The Drum is a good way to get yourself fixed up with a great little percussion synthesizer that can do all the fascinating things that you're hearing on the radio and TV (and much more), without going into the red. The Drum is a four-channel synthesizer consisting of four type-5700 percussion modules.

The Drum has some goodies that don't seem to be available on most percussion synthesizers now on the market. Let's examine the functions of some of the control and interface features on The Drum, and I think you'll see what I mean.

One of the most unique features of The Drum is its sensor device. It's a small audio transducer that can be mounted just about anywhere you want to put it. That means that you don't have to add more "things to hit" to your existing drums. You can simply mount the sensor on one of the drums you are already using and have that drum serve a dual purpose. The Drum synthesizer has provisions for a "cancel" control, such as an ordinary on/off type foot-switch (like the kind used with special-effects for guitar). That way, you don't have to dislocate your arm trying to hit a new piece that's behind you because there was no more room in front or to the sides.

For those who would like something that looks and feels like an actual drum surface, we have found that mounting the sensor in a practice-pad gives good results. However, it has also been noted that the dynamic range (evidenced by differences in synthesizer output pitch and volume level, with respect to the degree of force exerted on the practice-pad or drumhead) is somewhat less when using a practice-pad than that afforded by, say, a tom-tom. The reason is that the tom-tom (and just about any other drum) has a much longer decay time than a practice-pad, and a natural amplification that far exceeds that of the practice-pad. This gives the "envelope follower" circuit in the synthesizer a stronger and longer lasting signal to work with. We'll get into that a little later.

Since there are as many different ways to mount the sensor as one can think of, there must be a control on the synthesizer to allow the drummer to make adjustments for the differences in source-signal amplitude that will be encountered when using various drums and/or practice-pads as the "trigger" source. That control is simply a 500K pot, across which the input signal is dropped. The wiper picks off the desired signal level and feeds it to the input amplifier. We call that control SENSOR GAIN, and it is labeled R1 on the schematic in Fig. 1. The power supply for The Drum is shown in Fig. 2.

turn page for diagrams

Other front-panel controls include: ENVELOPE DECAY TIME, INITIAL PITCH, PITCH MODULATION UP/DOWN (this one is unique; we'll see why shortly), WAVEFORM SELECT/MIX, NOISE/OSCILLATOR MIX, NOISE FILTER (auto sweep or manual), and OUTPUT LEVEL. There are two status-indicator LED's on the front panel, one of them to show when the power is on, and the other to show when a trigger has been sensed.

We will explain the function of all those, as well as the half dozen interface jacks that are associated with The Drum module, in the design analysis.

How it works

The Drum transducer, which converts the mechanical action of striking the drumhead to the electrical input required by the synthesizer board, consists of a piezoelectric element encapsulated in a silicon compound. The silicon encapsulant supports and protects the element as well as serving as a coupling medium for the mechanical excitations. The voltage produced by the transducer is proportional to the magnitude of the mechanical force applied, (how heavily the drumhead is struck.)

The signal that is derived from the transducer is fed to input jack J1 (Fig. 1) and dropped across R1. The wiper of that pot picks off the signal at the desired level and feeds it to the non-inverting amplifier built around IC1-a; in turn, the amplifier

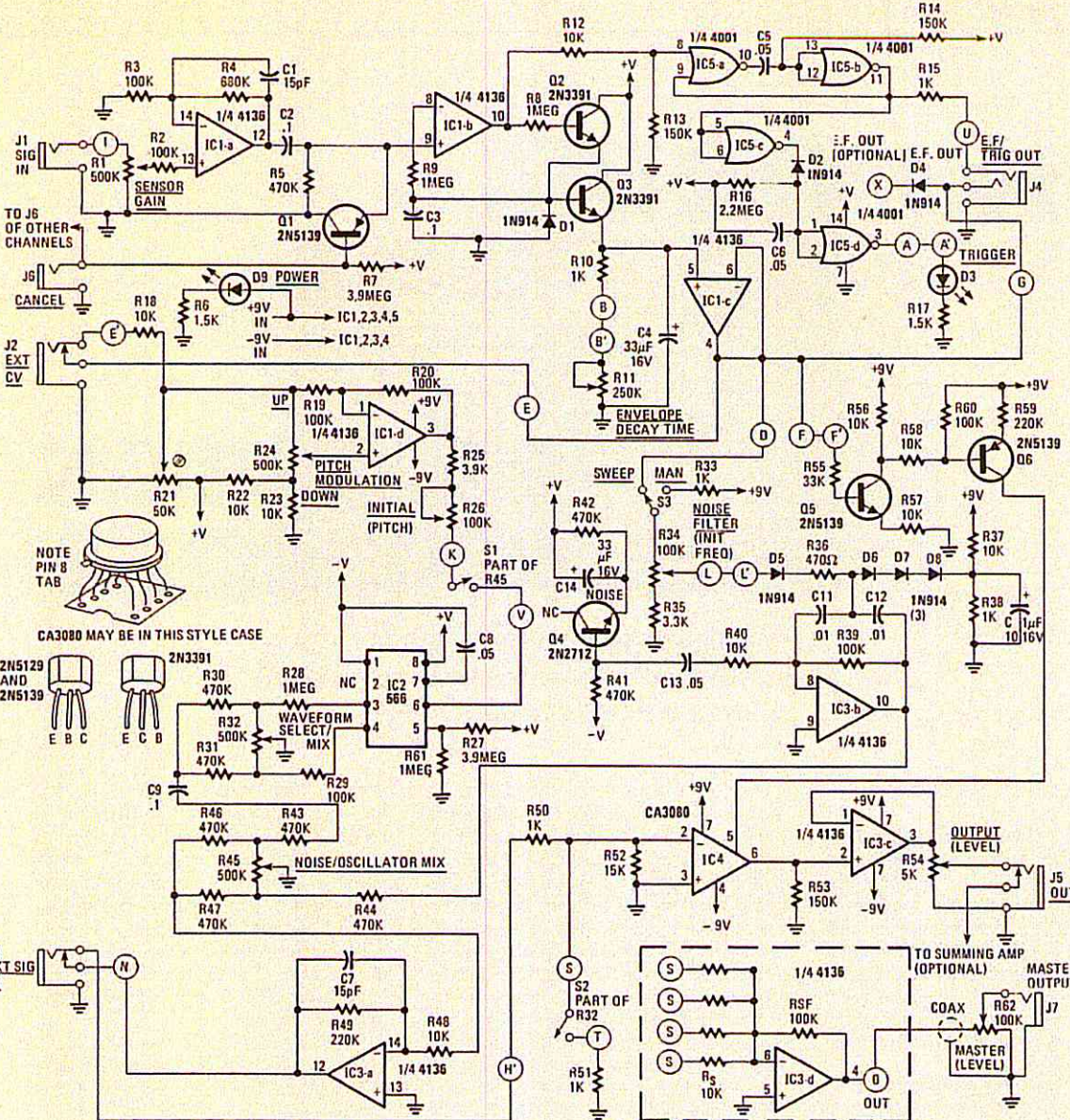


FIG. 1—SCHEMATIC DIAGRAM of the 5700 percussion-synthesizer module—the heart of drum synthesizer. Four of these modules are combined in the instrument shown in the photographs.

is capacitance-coupled to the next stage by C2.

Transistor Q1 allows a contact-closure to ground to serve as a cancelling function. Resistor R7 keeps this transistor's base positive so that it will remain in an off state under normal conditions. By grounding Q1's base through J6, any positive-going transitions of the signal voltage at its emitter will forward-bias it into a conducting state, thereby shunting the signal to ground via Q1's collector. We are not concerned with negative-going portions of the signal as the following stage will simply ignore any voltage going

below ground.

The buffered output of the transducer is applied to the non-inverting input of opamp stage IC1-b, which, in conjunction with Q2 and associated components, forms an envelope-follower. In response to positive excursions of the input signal, the output of IC1-b goes positive. The emitter of Q2 follows that voltage and charges C3 until its voltage (which is the signal voltage that is applied to IC1-b's inverting input) matches the original signal voltage. Negative input-signal excursions, or in fact an input voltage that is less than the voltage currently appearing

on C3, cause the base-emitter junction of Q2 to be reverse-biased, effectively allowing C3 to float.

A second effect of having Q2 reverse-biased is to break IC1-b's feedback loop so that the opamp functions most of the time as a comparator, its output (pin 10) switching between positive and negative supply. When pin 10 switches high, it triggers the monostable one-shot, composed of IC5-a and IC5-b; that produces a single short-duration pulse which is made available at the trigger-output connector of J4. That same short pulse is stretched by the circuitry of IC5-c and IC5-d and used to light the trigger-indicating light-emitting-diode, D3.

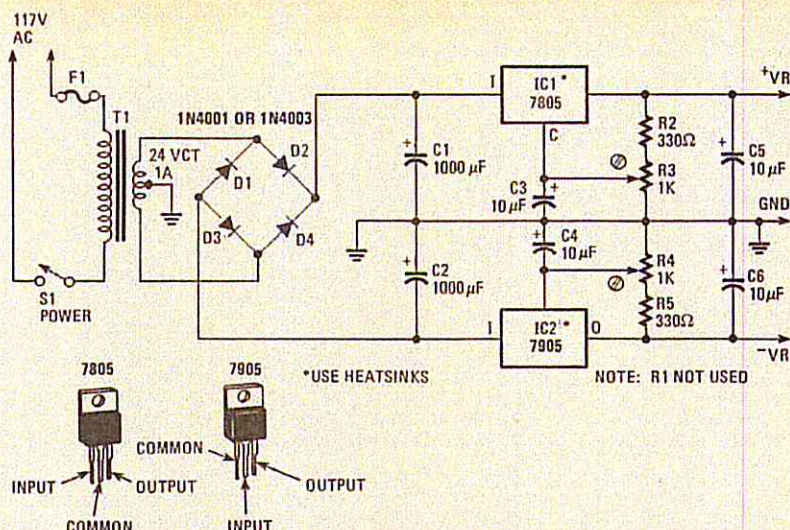


FIG. 2—THE POWER SUPPLY is hefty enough to supply the four modules that are used in the four-channel percussion synthesizer.

PARTS LIST

Resistors 1/4 watt, 10% unless otherwise specified

R1, R24—500,000 ohms, potentiometer, linear taper
 R2, R3, R19, R20, R29, R39, R60, R_{5F} (only one needed)—100,000 ohms
 R4—680,000 ohms
 R5, R30, R31, R41, R44, R46, R47—470,000 ohms
 R6, R17—1500 ohms
 R7, R27—3.9 megohms
 R8, R9, R28, R61—1 megohm
 R10, R15, R33, R38, R50, R51—1000 ohms
 R11—250,000 ohms, potentiometer, audio taper
 R12, R18, R22, R23, R37, R40, R48, R56, R57, R58, R₅ (only four needed) 10,000 ohms
 R13, R14, R53—150,000 ohms
 R16—2.2 megohms
 R21—50,000 ohms, trimmer potentiometer
 R25—3900 ohms
 R26, R34—100,000 ohms, potentiometer, reverse audio taper
 R32, R45—500,000 ohms, potentiometer, linear taper with SPST switch
 R35—3300 ohms
 R36—470 ohms
 R49, R59—220,000 ohms
 R52—15,000 ohms
 R54—5000 ohms, potentiometer, linear taper
 R55—33,000 ohms
 R62—100,000 ohms, potentiometer, audio taper (only one needed)

Capacitors

C1, C7—15 pF, ceramic disc
 C2, C3, C9—0.1 μF, Mylar
 C4, C14—33 μF, 16 volts or higher, electrolytic
 C5, C6, C8, C13—.05 μF ceramic disc
 C10—1 μF, 10 volts, electrolytic
 C11, C12—.01 μF, polyester

Semiconductors

D1, D2, D5—D8—1N914 or 1N4148
 D3, D9—TIL-209-B light-emitting diode
 Q1, Q6—2N5139 or PN5129
 Q2, Q3—2N3391 (GE)
 Q5—2N5129 or PN5129

Q4—2N2712 (GE, Sprague or other, selected for noise output. As supplied in the kit, the center lead has been clipped off.)

IC1, IC3—4136 quad op-amp (Exar, Raytheon, TI)

IC2—566 voltage-controlled oscillator (National, Signetics)

IC4—CA3080 (RCA or equal) operational transconductance amplifier

IC5—CD4001 CMOS quad NOR gate

S1, S2—SPST switch, on R32 and R45, respectively

S3—SPST slide switch

J1, J6, J7—open-circuit phone jack, 1/4 inch

J2, J3, J5—closed-circuit phone jack, 1/4 inch

J4—stereo phone jack, 1/4 inch

Miscellaneous: wire, knobs, hardware, circuit board, front and rear panels, drum transducer, etc.

The following are available from Paia Electronics, Inc., PO Box 14359, Oklahoma City, OK 73114:

No. 5700—Complete kit of all parts necessary for a single drum module, including drum transducer, circuit board, front panel, etc. \$59.95 plus \$3.00 postage and handling.

No. 5700PC—Etched, drilled and labeled circuit board for single module. \$15.95 postage paid.

No. 5700P—Complete kit for four-module drum set, including case, power supply, and four drum modules. \$269.75 plus \$10.00 postage and handling.

No. 5700S—Piezoelectric transducer \$25.00

No. 4771—Complete kit of parts for power supply \$29.95

No. 4771PC—Etched and drilled circuit board for power supply, \$6.95

Assembled units available. Write for prices.

POWER SUPPLY PARTS LIST

R1—not used
 R2, R5—330 ohms, 1/2 watt
 R3, R4—1000 ohms, trimmer pot
 C1, C2—1000 μF, 20 volts, electrolytic
 C3—C6—10 μF, 10 volts, electrolytic
 D1—D4—1N4001 or 1N4003
 IC1—LM340T-5 or 7805 positive voltage regulator, 5 volts
 IC2—LM320T-5 or 7905 negative voltage regulator, 5 volts
 T1—transformer, 24 volts, CT, 1 amp

Transistor Q3 serves as a second emitter-follower which tracks the voltage on C3 and provides the relatively heavy currents required to charge C4 quickly enough to produce a percussive attack waveform. Capacitor C4's discharge path is through resistor R10 and DECAY control R11. The attack and release (A/R) waveform that appears across C4 is buffered by the voltage-follower IC1-c. IC1-c's output provides the voltage that will control dynamics by means of the voltage-controlled amplifier and sweep the voltage-controlled oscillator and voltage-controlled filter.

Amplifier-stage IC1-d is configured as a sign-changer which allows the A/R control voltage to produce either upscale or downscale pitch shifts from the VCO. After it has been processed by the sign-changer, that control voltage is coupled by R25 and the INITIAL PITCH control R26 to the frequency-control input of the VCO, IC2.

The outputs of the 566 VCO are found at pins 3 (squarewave) and 4 (triangle). Because of the differences in the energy content of a squarewave and a triangle, the squarewave will sound louder. That accounts for the rather large difference between the values of the mixing resistors R28 and R29. The 500K pot R32 serves as a mix control by attenuating the unwanted waveform to the desired degree. Isolation-resistors R30 and R31 sum the mixed signal which is then coupled to the input of the next mixing stage by C9.

Resistor R43 couples the selected or mixed VCO signal to the VCO noise mixer circuit. The other input to this mixer circuit, R44, is fed from IC3-b. IC3-b's output is filtered white noise, generated by Q4—a transistor selected for its noise characteristics when operating in an avalanche condition.

The noise generated by Q4 is picked off at its base and capacitively coupled to the filter/amplifier IC3-b. Diodes D5, D6, D7, D8, and associated components, form the circuitry which sets the corner frequency of that filter. If S3 is switched to make connection with R33, then R34 (INITIAL FREQUENCY) serves as a manual filter frequency control. With S3 switched to sweep (the envelope follower output) the filter will be swept by the envelope-follower output and R34 serves as a sweep-range control.

DRUM SIMULATOR OR PERCUSSION SYNTHESIZER?

JOHN S. SIMONTON, JR.

ELECTRONIC CIRCUITS FOR SIMULATING drum sounds have been around for a long time. In the past they have primarily been simple bridged or parallel T oscillators as shown in Fig. 1. In use, the gain of the amplifier is adjusted so that the circuit is held just below the point of oscillation. When a narrow pulse is applied to one of those oscillators, its normal stability is disturbed and it generates a damped sinusoidal waveform.

That type of circuit is frequently used in automatic percussion units because in that kind of application we are most concerned with the timing of the beats.

The reason that every drummer in the world is not rushing out to replace his bulky and cumbersome instruments with those small, inexpensive electronic equivalents is that devices of that type aren't capable of the dynamic control that a musician needs for personal expression in performance. Damped oscillators are good for simulating the sound of a fixed-pitch drum struck with more or less constant force, but little else.

But recently, many percussionists have begun to use electronics to supplement their traditional instruments, using devices that can capture the dynamics and style of their playing. And because the circuitry used in these electronic drums is close kin to that used in modern electronic music synthesizers, drum synthesizers can produce an unbelievably wide range of voices from natural to unearthly.

Figure 2 shows a block diagram of a typical drum synthesizer (The Drum, as it happens). Undoubtedly the most striking difference between that and a more conventional type of music synthesizer is that The Drum has no keyboard, this element's function of real time control being taken over by the drum transducer, a device that translates the force of the stick hitting the drumhead into an electrical signal that the rest of the synthesizer can use.

After being amplified, the output of the transducer is applied to a circuit that is called an envelope follower, but is in fact more a peak detector with a controllable release time. The envelope produced by this circuitry is used in a number of ways. In conjunction with the voltage-controlled amplifier it is used to change the constant amplitude output of an oscil-

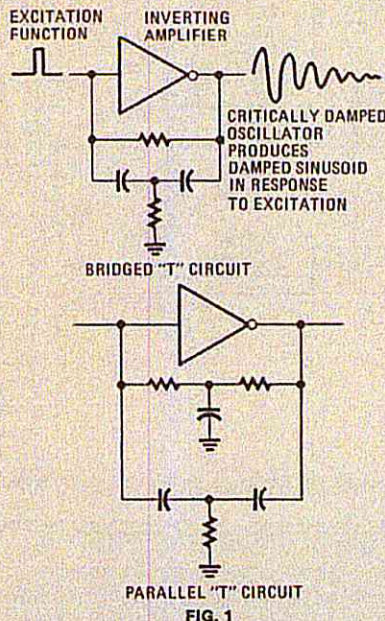


FIG. 1

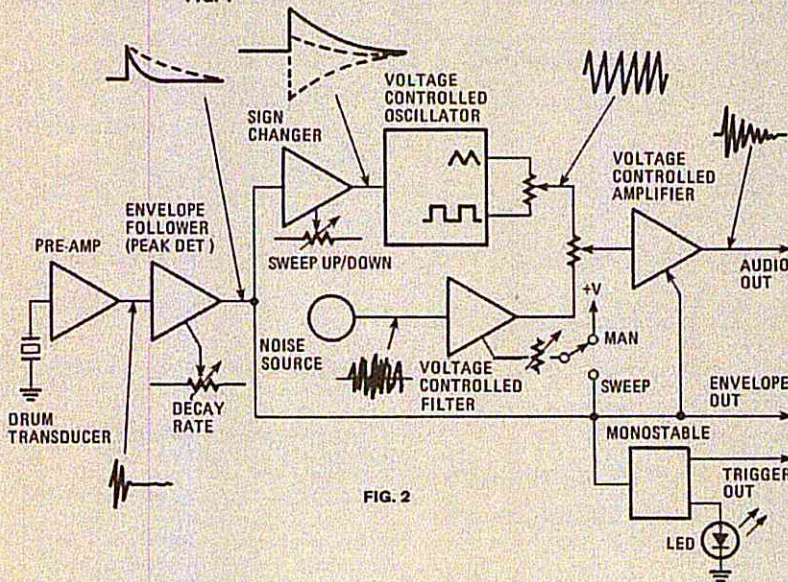


FIG. 2

lator into the classic percussive sound envelope. That approach is capable of producing longer decay times than are possible with either mechanical drums or damped oscillators. And since the peak output of the envelope follower is related to the output of the drum transducer, which is in turn a function of the striking

force, dynamics are preserved.

The control envelope is also applied to a sign changer where it can be either attenuated or inverted depending on the setting of a knob and the resulting new control voltage is used to change the frequency of the primary pitch source, a voltage-controlled oscillator. Because of that the pitch can be modulated either up or down to follow the envelope (like a pedal timpani only with much greater than natural range); or, at mid settings of the control, produce no pitch shift at all.

The use of a VCO as the pitch source also allows us a somewhat broader selection of the tone colors than is allowed by alternative expedients.

In addition to a pitched component, many drums—most notably snares—also have un-pitched components. In the synthesizer, un-pitched sounds are produced by the noise source. Since noise comes in different colors (white, pink, etc.), a voltage-controlled filter is provided to alter the noise spectrum as desired. The filter

is voltage controlled so that it too can track the envelope, another effect that can not be duplicated by mechanical drums.

The remaining circuitry (envelope and trigger out, etc.) is useful in combining more than one synthesizer card to produce a single voice.

Resistor R45 works in a manner similar to R32 in the waveform-mix circuit, attenuating either signal to the desired degree. Resistors R46 and R47 sum the mixed signal and feed it to the input of the buffer amplifier IC3-a and from that point the signal is applied to the signal input of the VCA, IC4.

Except when sinewave output is select-

ed, S2 will be closed, putting R51 in parallel with R52. That provides an attenuator at the input of IC4 which will keep the input signal level to the CA3080 transconductance amplifier within its linear operating region (input of 100 mv or less). Opening S2 removes the major portion of the attenuator and allows the VCO triangle output to overdrive the VCA's

input slightly, producing a sinewave.


The gain of IC4 is determined by the current that is flowing into pin 5 of the device. That current flow is manipulated by Q5 and Q6 which in turn are controlled by the envelope-follower's A/R output voltage.

We'll discuss construction and use next month.

R-E

BUILD THIS

the DRUM...

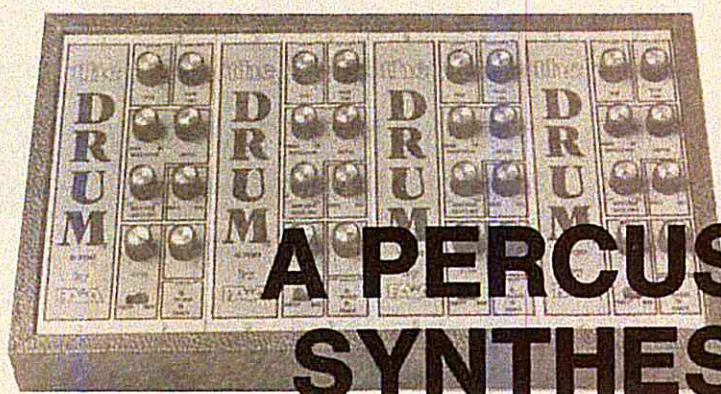

A PERCUSSION SYNTHESIZER

Part 2—Full construction details as well as a detailed description of the operating controls are given in the conclusion of this project.

STEVE WOOD

LAST MONTH WE DISCUSSED THE DRUM and its theory of operation. Now, we'll go into construction. Remember that the four-channel instrument described and shown in the photos is composed of four identical drum-synthesizer modules. Although the four modules are basically identical, the summing circuit and summing amplifier are installed only on the board for channel four. The power-supply foil pattern and parts-placement diagram are in Figs. 3 and 4, respectively.

The PC board for the synthesizer modules is laid out with ease of assembly in mind. Its foil pattern is shown in Fig. 5 and parts-placement details are shown in Fig. 6 and the photo in Fig. 7. Note that everything except the six input and output jacks is mounted on the circuit board. Be sure to give the foil side of the board a cleaning before starting assembly.

Install all the passive components first, starting with the resistors, then capacitors and jumpers. Next, mount the control pots, slide switch, and the two LED's—installing them on the foil side of the board. Figure 8-a shows details of the mounting of those parts on the foil side of the board. The control pots are mounted by soldering their lugs to the pads on the PC board. The body of the pot goes into a hole that is an exact fit. The bottom of the pot is flush with the component side of the board. Pots R32 and R45 are exceptions since they have switches on them.

See Fig. 8-b. Fig. 9 shows the front panel of one of the modules.

When installing slide switch S3 (Fig. 8-c), you must insulate its case from the copper foil on the PC board. Thin foam

tape is ideal for the job but ordinary black electrician's tape will do. It should be placed just under the switch case, along the sides of the holes that the switch lugs will pass through.

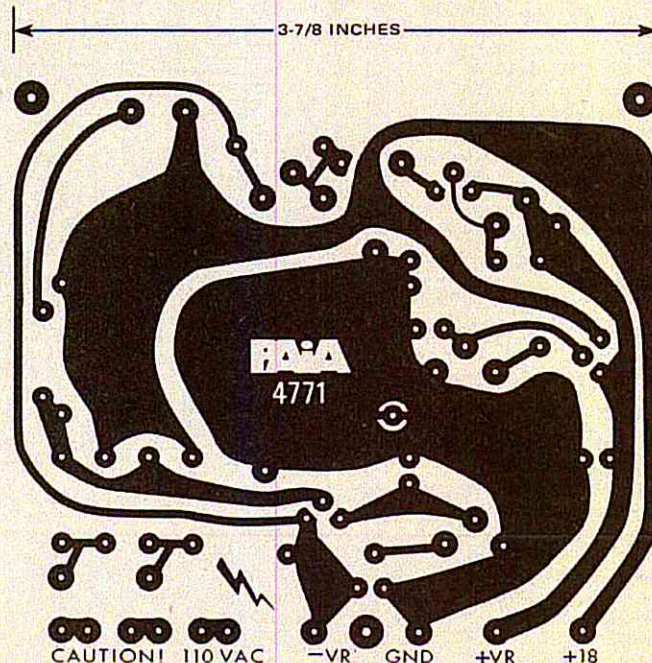


Fig. 3—FOIL PATTERN for the power supply. The power transformer is mounted on the bottom of the case, in the left-rear corner next to the supply circuit board.

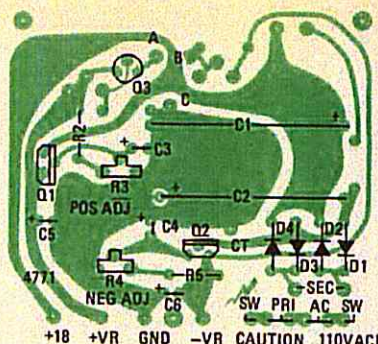


FIG. 4—POWER-SUPPLY PARTS-PLACEMENT GUIDE. The supply circuit has been simplified so some pads and circuit leads are not used.

The LED's are inserted in holes in the front panel. The panel is $\frac{1}{4}$ -inch aluminum, so alignment can get a bit tricky. It helps to crimp the leads on each LED so that when you install the panel you can work the LED's up through the holes as the panel is being set down over the bushings of the pots.

Number 22 hookup wire and some good small-diameter coaxial cable is used in making the connections between the PC board and the jacks. Figure 10-a shows how the jacks are wired. Use bare wire to connect the ground lugs (lug 2) on each jack. Start with J1, forming a small hook and anchoring the wire in lug 2. Roughly measure the distance to lug 2 on J3 and cut a piece of plastic insulated sleeving (spaghetti) to that length. Slip the tubing over the wire and pass it through lug 2 on J3. Continue around through J6, J4, J2, and J5, insulating the common ground lead between all ground lugs. Solder the connections at J5 and J6 only.

Run single-conductor wires from indicated pads on the circuit board to the proper lugs on the jacks. You will have leads from points C, E, E', G, and U. Now, following Fig. 10-a, run lengths of coax cable from the circuit board to the jacks. Note that the shield braid always connects to a ground lug (lug 2). Wire S1, J7 and R62 as in Fig. 10-b.

When you get the four modules wired and installed in the cabinet, and wired up, turn on the power and carefully check the voltages. You'll have +9 volts at 20 mA, -9 volts at 20 mA and the POWER indicator LED should light. The TRIGGER indicator LED should flash when you strike the transducer.

Calibration

This step is a snap! Just set the controls up like this:

SENSOR GAIN	approx. 3 or 4
DECAY TIME	approx. 3 or 4
PITCH MOD.	fully CCW (down)
INITIAL PITCH	approx. 3 or 4
WAVEFORM	sine (fully CCW past detent)
MIX	osc. (fully clockwise)
NOISE FILTER	fully CCW
SWEEP/MAN	manual
OUTPUT	Midway (adjust as required)

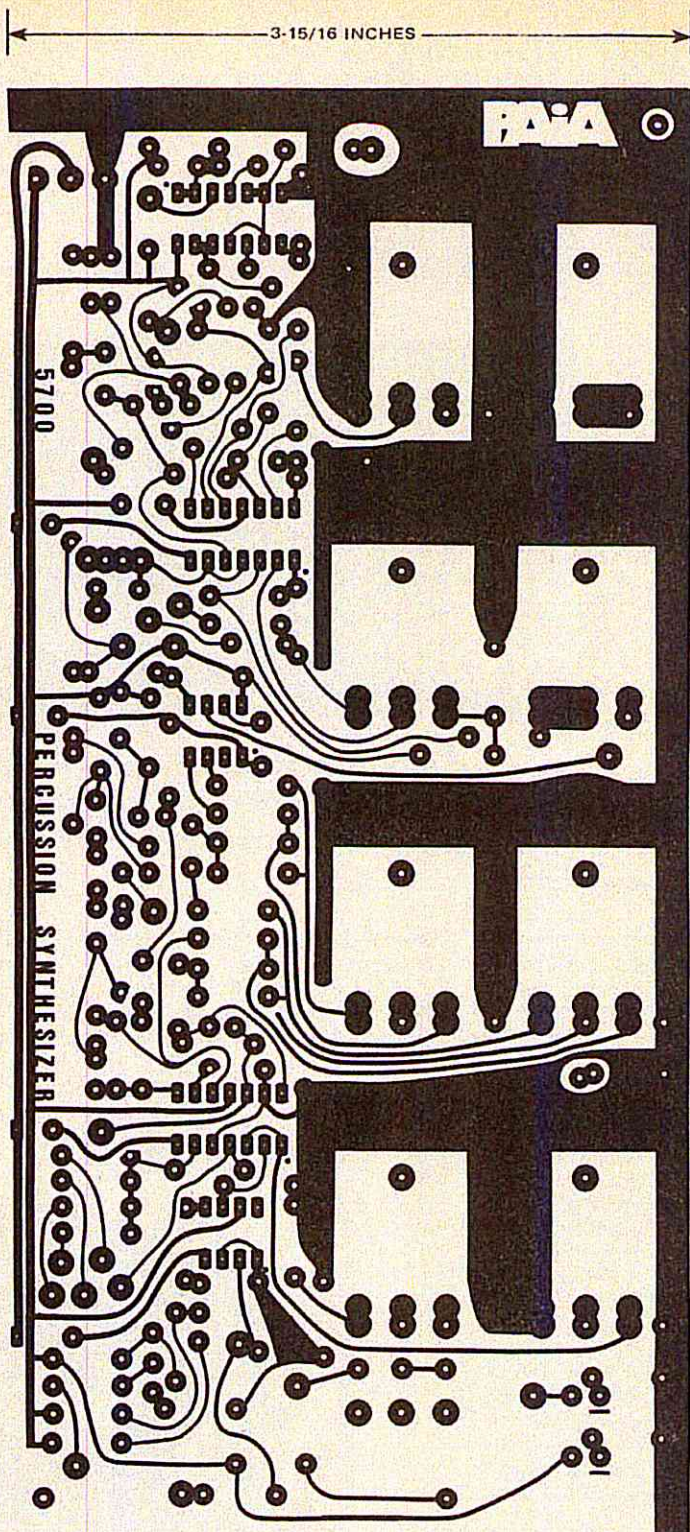


FIG. 5—PATTERN for one drum-synthesizer module. You need four modules to duplicate The Drum.

Now, strike The Drum transducer with a pencil or your finger. You should hear the pitch go down in frequency and die out in a short time.

Trigger The Drum several more times and play with the DECAY TIME control. Note that as the control is rotated farther

clockwise, the downward sweep in pitch becomes slower and it takes longer for the tone to become inaudible. Leave the DECAY TIME control set at some intermediate value.

Rotate the MODULATION control from DOWN to UP. Notice that as the control is

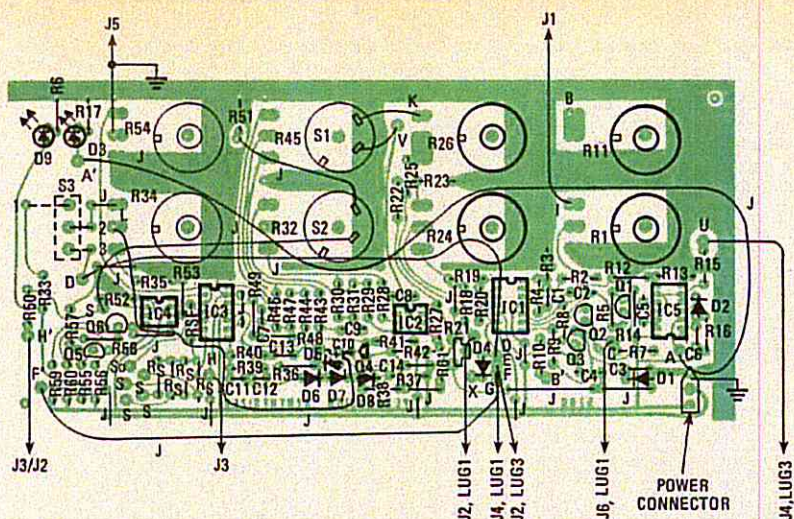


FIG. 6—HOW PARTS ARE POSITIONED on the synthesizer modules. The four R_8 resistors are installed only on the module for the fourth channel. The diagram also shows jumpers and connections to off-board components.

rotated, the amount of downward pitch shift as The Drum sounds decays decreases until at some position of the control there is no pitch shift at all. Further clockwise rotation beyond this point should cause the pitch to shift up.

Set the internal trimmer R21 as follows: Rotate the MODULATION control fully CCW (DOWN), trigger the Drum and make a mental note of the pitch produced at the beginning of the downward sweep. Next turn the MODULATION control to fully CW (UP), and once again trigger The Drum. Adjust R21 so that the pitch produced at the end of the upper sweep closely matches the pitch at the beginning of the previous downward sweep. This is not a critical adjustment and may be set to taste.

Turn the INITIAL PITCH control in the clockwise direction and observe that the output pitch increases as the control is rotated. Return the control to a setting of 3 or 4.

Switch the WAVEFORM MIX control to the triangle position, just clockwise from the detent. When The Drum is triggered now, you should be able to hear a slight, but noticeable difference in the timbre, as the output changes from a sine wave to the selected triangle. If you can't tell any difference, try turning the OUTPUT level control down some and turn your amplifier volume up to compensate. As the WAVEFORM MIX control is rotated in a clockwise direction from triangle to square wave, the timbre should become progressively less "mellow." Return the WAVEFORM MIX control to the sine position.

While triggering The Drum, begin rotating the NOISE/OSC MIX control in a counterclockwise direction toward the NOISE position and observe that progressively more noise is mixed into the output. Rotate the control fully CCW past the detent and note that there is only noise in the output and no oscillator signal is present at all.

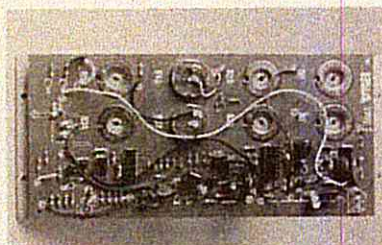


FIG. 7—REAR-VIEW of one of the modules. Use it along with Fig. 6 when you are placing parts and jumpers.

With the NOISE/OSC MIX control set fully CCW, continue triggering The Drum and observe that rotating the NOISE FILTER control clockwise causes apparent pitch of the noise to increase.

With the NOISE/FILTER control set to its mid-range position, change the SWEEP/MAN switch to its SWEEP position and note

that the apparent pitch of the noise now follows the drum envelope. Also observe that with the filter in the sweep mode, the FILTER control is acting as an initial frequency control which increases the "range" of the filter sweep as the control is rotated CW.

Using the drum

The DRUM has a number of front-panel controls (Fig. 9) and jacks (Fig. 10) on the back panel. While some of them follow conventional designs, others offer control features or interface capability not found on many other percussion synthesizers. The following is a list of those controls and connectors, and a brief description of their function:

SENSOR GAIN—This control sets the sensitivity of the 5700 to the triggering signal from the sensor. If it is set too high The Drum will trigger too easily, resulting in false triggering and loss of dynamic range. Too low a setting will make The Drum hard to trigger.

ENVELOPE DECAY TIME—This control sets the decay time. The decay time becomes longer as the control is rotated clockwise.

INITIAL PITCH—This control sets the initial pitch of the VCO, which constitutes The Drum pitch source. Clockwise rotation of the control increases the initial pitch.

MODULATION UP/DOWN—This control, when set fully counterclockwise (to DOWN) causes a downward sweep of the pitch source. Full clockwise rotation (to UP) makes the pitch sweep up after triggering. Settings between those two extremes produce progressively less pitch modulation, and when the control is centered there should be no pitch modulation at all when The Drum is triggered.

WAVEFORM SELECT/MIX—This control

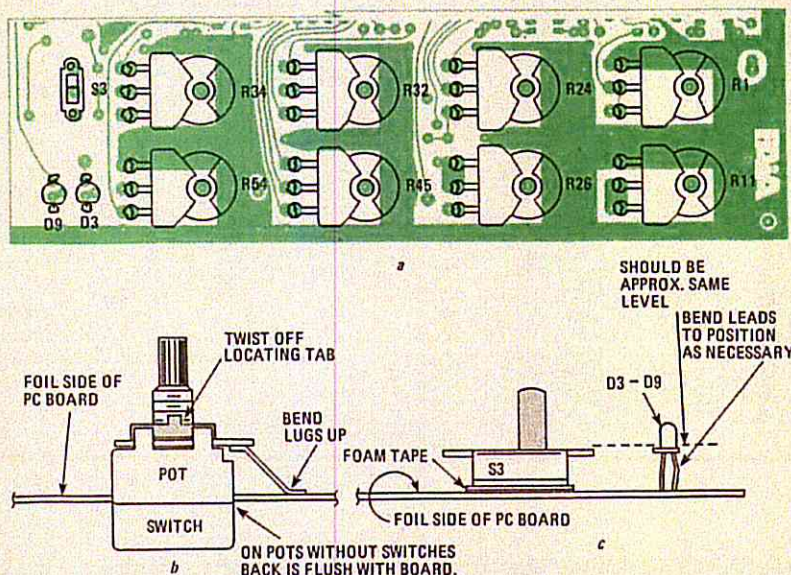


FIG. 8—HOW POTS, SWITCH, AND LED's are mounted on the PC board. Diagram at a shows how potentiometer lugs are soldered to pads on the PC board. Sketch at b shows how to shape the control lugs before soldering and c shows details of switch S3 and LED mountings.

allows mixing of waveforms from the VCO. Turned fully counterclockwise, past the detent, the output signal will be a sine wave. Turning the knob in a clockwise direction just past the detent produces a triangle waveform. Continued clockwise rotation of the control begins to mix a square wave into the output until at the extreme end of the rotation the signal is completely square wave.

NOISE/OSCILLATOR MIX—This control provides mixing between the VCO signals and filtered white noise. Full clockwise rotation will produce VCO signal only. Full counterclockwise rotation past the detent will produce an output signal

of noise only. Positions between these extremes will cause the output to be a mix of both pitched signal and noise.

SWEEP/MAN—This slide switch allows the corner frequency of the filter associated with the noise source to either track the drum envelope (in the SWEEP position) or to be set to a fixed value (MAN position).

NOISE FILTER—This control sets the corner frequency of the filter when the SWEEP/MANUAL switch is in the MAN position and sets the sweep range of the filter when the switch is in the SWEEP position.

STATUS—There are two LED's on The Drum front panel. The LED labeled POWER should continuously light any time power is applied to the PC board. The TRIGGER-indicating LED will wink briefly at each triggering of the synthesizer circuitry.

OUTPUT LEVEL—Clockwise rotation increases output signal level.

Back panel jacks

J1 (INPUT)—This jack is the input from which The Drum synthesizer derives dynamics information (when and how hard the drum was struck). The input can come from the drum transducer or from a microphone or other audio transducer. For computer interface, this input can come from a digital-to-analog converter.

J2 (EXT CV IN)—This jack is an external control voltage input. When a control voltage source is plugged into this jack the envelope-follower output will be disconnected from the VCO frequency controlling circuitry and the external source will take its place. Both UP/DOWN MOD. and INITIAL PITCH controls will still be functional.

J3 (EXT SIG IN)—This jack is used to apply an external audio source directly to The Drum's VCA for percussive voicing. When used, this jack will disconnect the internal signals from the VCA and only the external signal will be passed. Unless

working with extraordinarily high external signal levels, the WAVEFORM SELECT/MIX control should be kept in the sine position.

J4 (E.F./TRIGGER OUT)—This is a stereo jack that carries two output signals. On the ring or collar connector (lug 3) is the trigger output which goes high briefly each time The Drum is triggered and on the tip connector (lug 1) is a time-varying DC voltage which is the output of the A/R generator. There are numerous possible uses for those signals; for example, the envelope of one 5700 card can be routed to the EXT CV IN of a second card and the two outputs mixed to produce a dual-oscillator drum voice. To operate two drums from one sensor, take EF/OUT signal from point "X" and feed it to J1 of the second drum module.

In computer applications, the TRIGGER OUT can be used to signal the processor that the drum has been struck while the E.F. OUT is connected to an analog-to-digital converter (such as the PAIA EK-7 Dual Digitizer) to provide dynamics information in a digital form.

J5 (OUT)—This is the audio output jack. It is a closed-circuit jack that will pass the output signal to a summed output in a multi-channel system when no plug is inserted.

J6 (CANCEL)—A switch plugged into this jack will allow for disabling The Drum when not required. This is particularly useful when using the synthesizer with an existing drum set. Connect the four CANCEL jacks in parallel and then you can control the four channels with one footswitch.

Some good friends played around with a rough four-channel prototype while The Drum was under development. A surprising number of options were discovered in relation to the mounting of the transducer ranging from gluing it to an externally-mounted muffler to the obvious (taping it to the bottom of the drum head). Actually, you can put the transducer anywhere you want to: on the inside of the drum shell, or on the outside of that matter, or on a bottom head—if you have them. It doesn't care! A convenient means of temporarily mounting the sensor while searching for just the right place is to use a foam tape with adhesive on both sides. The actual mounting details will depend on your personal preference. Before you decide on a particular location, move the sensor around a bit. The results may surprise you. When the best sensor location is found, the transducer can be permanently mounted there with *Instant-Weld* or a similar adhesive. It also works out quite nicely to mount it in a practice pad (also available from PAIA).

If you don't have the transducer that's available from PAIA, you can get by with a high-impedance microphone (though The Drum's dynamic response may suffer).

R-E



FIG. 9—THE FRONT PANEL of the 5700 synthesizer module with the codes keyed to the various controls.

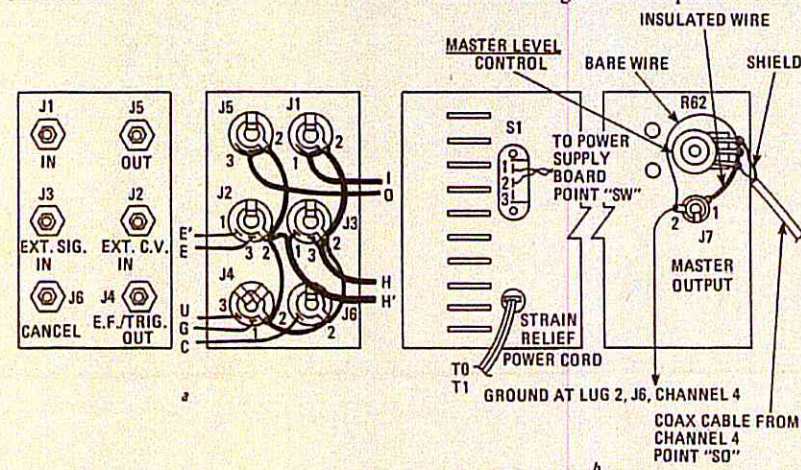


FIG. 10—HOW COMPONENTS ARE MOUNTED on the rear panel. Drawings at a show the jacks: how they are positioned and connected to coded points on the circuit board. Four sets of jacks are used—one set of six for each synthesizer module. The drawings at b show components on the ends of the rear panel.